

$$F = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

Draw a multiplexer with 4 variables and 1 selector bit

- Truth Table:


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- Karnaugh Map F_1

		C		
	0	1	1	0
B	1	0	0	0
	D			

$$F_1 = B'D + BC'D'$$

- Karnaugh Map F_2

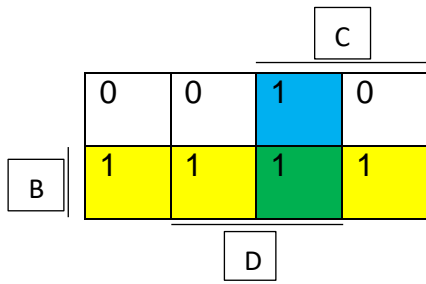

$$F_2 = B + CD$$

- Multiplexer

